



Sources are the pool of energy from where whatever amount of energy is extracted, the net energy in the pool remains same.

2 types of sources.

Voltage Source

- Batteries, Cell, Alternator

Current source

- Made electronically to deliver constant current.

LOAD (Resistance)

1) Voltage Source :-

- Internal Resistance of a Voltage Source.
- Internal Resistance of an ideal voltage source should be zero.
- Can be replaced by a short circuit.

2) Current Source

① Symbol

- Internal Resistance of an ideal current source must be ∞ .


Ohm's Law :-

$$i \propto V_A - V_B \quad (\text{Subject to Const. physical condition (temp)})$$


$$i \propto V \quad i = \frac{V}{R} \quad (\text{Const.} = \frac{1}{R})$$

$$V = iR$$

Linear Element \rightarrow

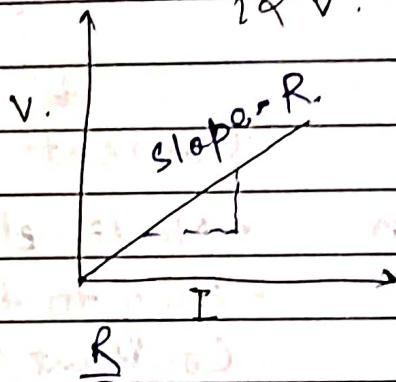


Bilateral Element \rightarrow

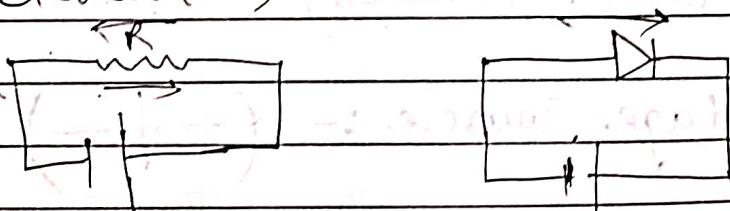

If the property of element should not change with change of direction.


KIRCHHOFF'S LAW

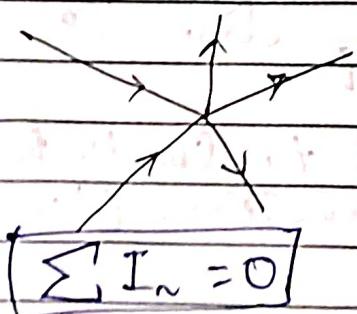- ① Kirchhoff's current law (KCL) \rightarrow In a linear bilateral closed circuit, the current entering a node/junction is equal to the current leaving the node/junction. $\sum i = 0$ (at a node/junction)




\rightarrow There is no accumulation of current at any node.

② Kirchoff's Voltage law (KVL).

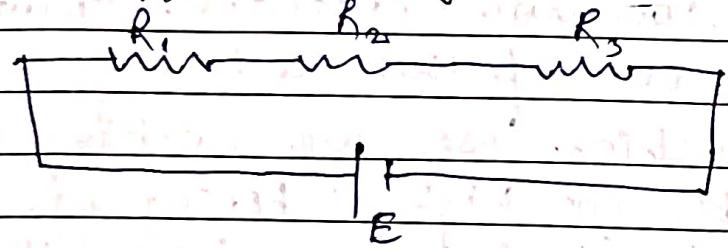

$$\sum E_n = \sum V_{drop}$$

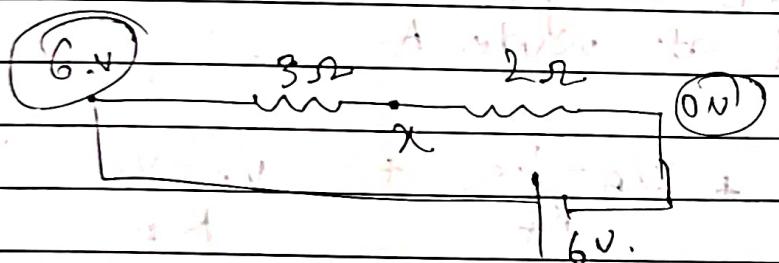

$$V_i = \frac{6 \times 3}{3+2} = \frac{18}{5}$$


→ In a linear bilateral network containing n no. of elements and m no. of sources the total potential applied is dropped on the elements.

$$V_{drop} = IR_1 + IR_2 + \dots$$

Method:-

① Node Voltage Method:

→ Application of KCL

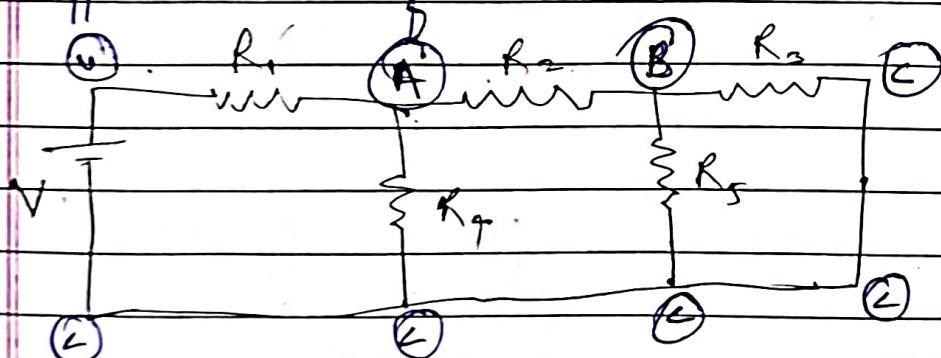


- ① Mark all the common Potential Points.
- ② Ground any one of the node.
- ③ the node on which we are working is assured to be at highest Potential.
- ④ All the currents flowing away from node a , taken as true and viceversa.
- ⑤ Then apply KCL to get the currents.
- ⑥ Applying KCL at node A

$$\frac{V_A - V_{\infty} - V_C}{R_1} + \frac{V_A - V_S}{R_4} + \frac{V_A - V_B}{R_2} = 0$$

- ⑦ Apply KCL at node B.


$$\frac{V_B - V_A}{R_2} + \frac{V_B - V_C}{R_3} + \frac{V_B - V_S}{R_5} = 0$$

$$I_1 = 3A$$

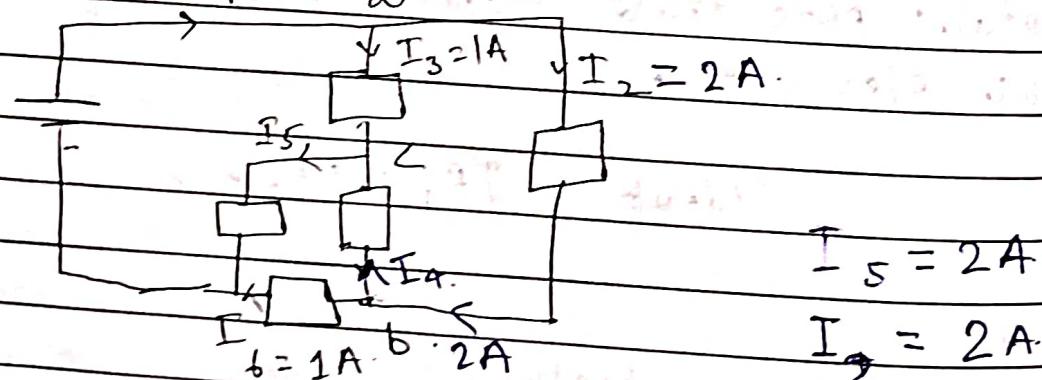

NODAL ANALYSIS

→ To apply KCL in circuits.

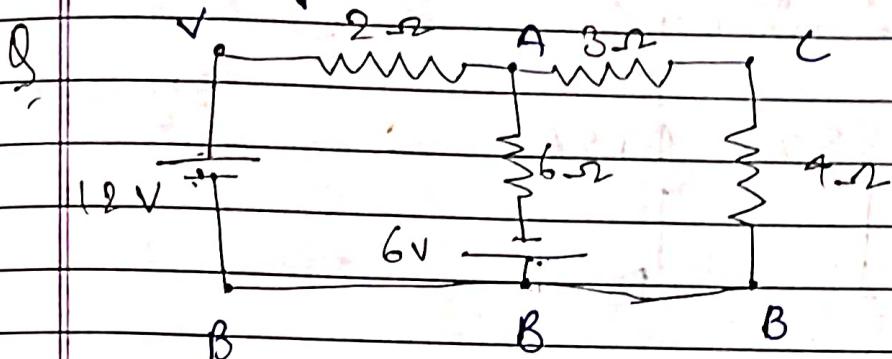

① Identify nodes (A & B).

② Ground node B.

$$\therefore V_B = 0.$$

③ Apply KCL at node A.

$$\cancel{V_B} \quad \frac{V_A - 12 - V_B}{2} + \frac{V_A + 6 - V_B}{6} +$$

$$\frac{V_A - V_B}{7} = 0$$

$$\left(\frac{V_A - V_B}{2} - 12 \right) + \frac{V_A - V_B + 6}{6} + \frac{V_A - V_B}{7} = 0$$

$$\frac{V_A - 12}{2} + \frac{V_A + 6}{6} + \frac{V_A}{7} = 0.$$


$$7V_A - 42 + 7V_A + 7 + V_A = 0.$$

$$15V_A = 42 \quad | :15 \quad i_1 =$$

$$V_A = \frac{42}{15} = 2.8 \text{ V}$$

$$V_A \left(\frac{1}{2} + \frac{1}{6} + \frac{1}{7} \right) = 5$$

$$V_A = 6.17 \text{ V}$$

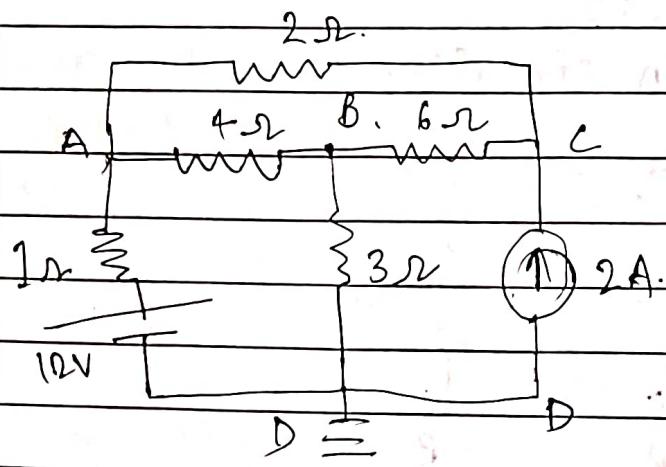

$$A \rightarrow \frac{V_A - 12}{1} + \frac{V_A - V_B}{4} + \frac{V_A - V_C}{2} = 0$$

$$B \rightarrow \frac{V_B - V_A}{4} + \frac{V_B - V_C}{3} + \frac{V_B - V_D}{2} = 0$$

$$C \rightarrow \frac{V_C - V_A}{2} + \frac{V_C - V_B}{6} = 0$$

$$0 = 3V - 2V$$

$$D \rightarrow 0 = 4V - 12V + 8V - 2V$$

$$0 = 4V - 12V + 8V - 2V$$

$$0 = 4V - 12V + 8V - 2V$$

$$0 = 4V - 12V + 8V - 2V$$


$$0 = 4V - 12V + 8V - 2V$$

$$0 = 4V - 12V + 8V - 2V$$

$$0 = 4V - 12V + 8V - 2V$$

Mesh / Loop current Method :-

for applying KVL.

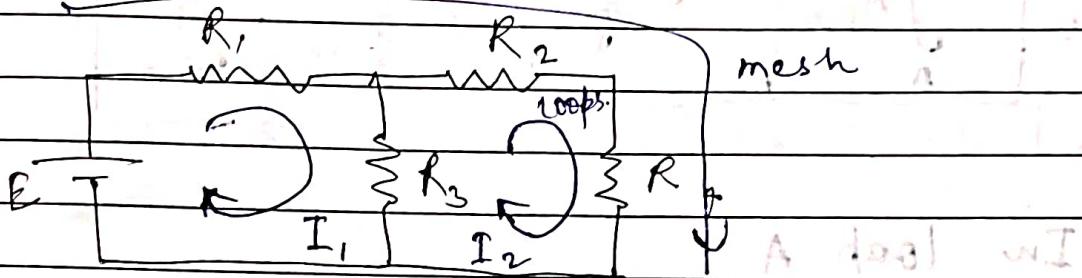

① Identify loop / mesh - (01 - 01)

② Battery or cell sign.


→ when current is coming out of the plate of cell the cell is discharged hence taken as -ve else +ve

③ Potential drop sign.

→ If we take moving in assumed dirn of current then the potential drop is taken as +ve else -ve

④ The loop in which we are working is assumed to carry max. value of current.

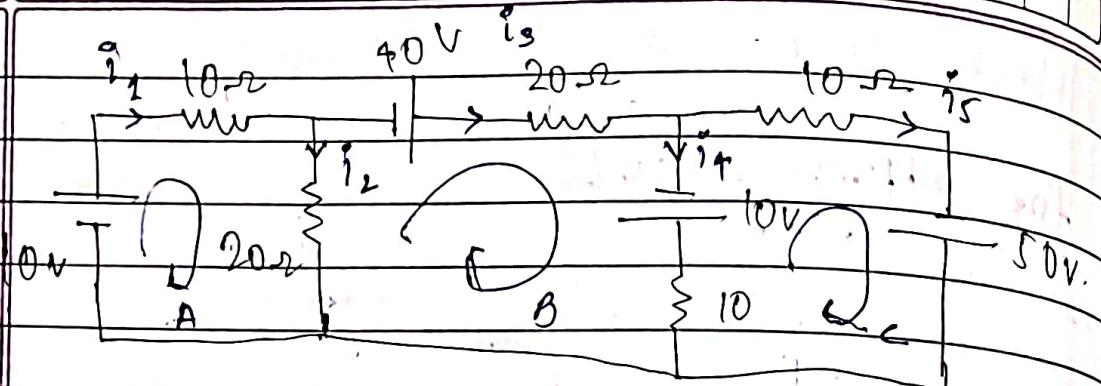Q Find current through all the resistances in the following circuit using mesh current method.



In loop A

$$10 - 10i_1 - 20i_2 = 0$$

In loop B.

$$40 - 20i_3 + 10 - 10i_4 - 20i_2 = 0$$

In loop C.

$$10 - 10i_4 - 50 + 10i_5 = 0$$

$$\Rightarrow 10 - 10i_1 - 20i_2 = 50 - 20i_3 - 10i_4 - 20i_5$$

$$20i_3 + 10i_4 - 10i_2 = 40$$

$$10 - 10i_1 - 20i_2 = 10 - 10i_4 - 50 - 10i_5$$

$$50 = 10i_1 + 20i_2 - 10i_4 - 10i_5$$

$$40 - 20i_3 + 10 - 10i_4 - 20i_2 = 10 - 10i_4 - 50$$

$$90 = 20i_3 + 20i_2 - 10i_5$$

$$40 + 10i_1 + 20i_2 - 10i_4 - 10i_5 = 11$$

$$120i_3 + 20i_2 - 10i_5$$

$$40 + 10i_1 - 10i_4 = 20i_3$$

(Y) loop

(Δ) node

$$Y \leftarrow \Delta$$

Δ is a Δ node containing resistors

$$(a_1 + a_2) \Delta R =$$

$$a_1 R + a_2 R$$

transformers are Y & Δ Δ

$$(a_1 + a_2) \Delta R = a_1 R + a_2 R$$

$$a_1 R + a_2 R + a_3 R = a_1 R + a_2 R + a_3 R$$

$$(a_1 + a_2 + a_3) \Delta R = a_1 R + a_2 R + a_3 R$$

$$a_1 R + a_2 R + a_3 R + a_4 R = a_1 R + a_2 R + a_3 R + a_4 R$$

$$(a_1 + a_2 + a_3 + a_4) \Delta R = a_1 R + a_2 R + a_3 R + a_4 R$$

$$a_1 R + a_2 R + a_3 R + a_4 R + a_5 R = a_1 R + a_2 R + a_3 R + a_4 R + a_5 R$$

100% parallel


$$a_1 R + a_2 R + a_3 R + a_4 R + a_5 R = a_1 R + a_2 R + a_3 R + a_4 R + a_5 R$$

$$a_1 R + a_2 R + a_3 R + a_4 R + a_5 R = a_1 R + a_2 R + a_3 R + a_4 R + a_5 R$$

(W) end result

$$a_1 R + a_2 R + a_3 R + a_4 R + a_5 R = a_1 R + a_2 R + a_3 R + a_4 R + a_5 R$$

Star - Delta Conversion

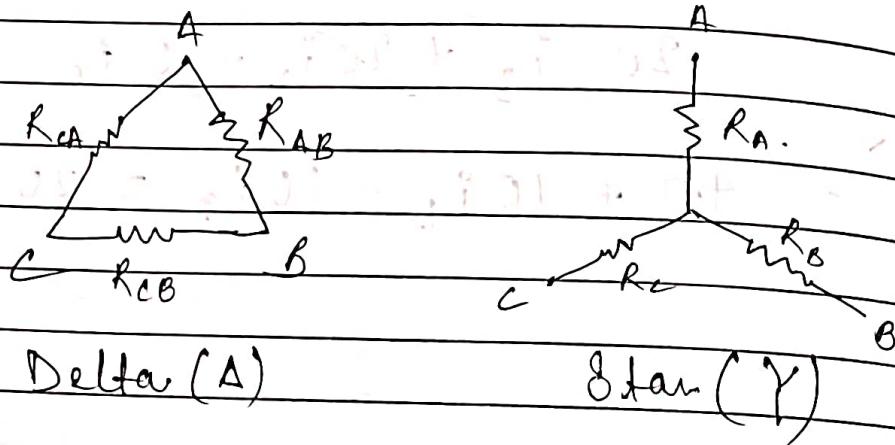

$\Delta \rightarrow Y$

Equivalent resistance b/w A & B in Δ
 $= \frac{R_{AB} (R_{BC} + R_{CA})}{R_{AB} + R_{BC} + R_{CA}}$

As Δ & Y are equivalent

$$\therefore R_A + R_B = \frac{R_{AB} (R_{BC} + R_{CA})}{R_{AB} + R_{BC} + R_{CA}}$$

$$\therefore R_B + R_C = \frac{R_{CB} (R_{AB} + R_{CA})}{R_{AB} + R_{BC} + R_{CA}}$$

$$\therefore R_A + R_C = \frac{R_{CA} (R_{AB} + R_{BC})}{R_{AB} + R_{BC} + R_{CA}}$$

Adding ① & ②

$$R_A + 2R_B + R_C = \frac{R_{AB} (R_{BC} + R_{CA}) + R_{CB} (R_{AB} + R_{CA})}{R_{AB} + R_{BC} + R_{CA}}$$

Now subs. ③.

$$2R_B = \frac{R_{AB} (R_{BC} + R_{CA}) + R_{CB} (R_{AB} + R_{CA}) + R_{AC}}{R_{AB} + R_{BC} + R_{CA}}$$

$$R_B = \frac{R_B (R_{AB} + R_{BC} + R_{CA})}{R_{AB} + R_{BC} + R_{CA}}$$


$$R_A = \frac{R_{AC} \times R_{AB}}{R_{AB} + R_{BC} + R_{CA}}$$

(i) x (ii) + (ii) x (iii) + (iii) x (i) will give.

$$R_{AB} = R_A + R_B + \frac{R_A R_B}{R_C}$$

$$R_{BC} = R_B + R_C + \frac{R_B R_C}{R_A}$$
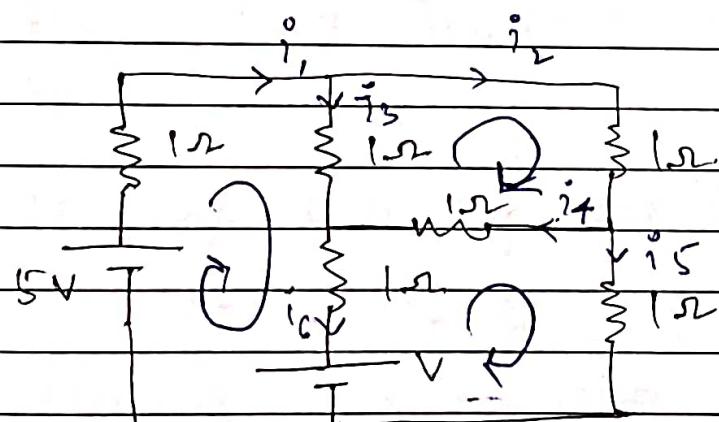
$$R_{CA} = R_C + R_A + \frac{R_C R_A}{R_B}$$



Applying KVL and find the value of V so that current through 5V is 0. → Applying KCL & find the value of V.

$$\rightarrow 5 - i_1 - i_3 - i_6 - V = 0$$

$$-i_2 - i_4 - i_3 = 0$$

$$V - i_6 - i_5 - i_3 = 0$$

$$5 - (i_1 - i_2) - (i_2 - i_2 - i_4) = 0$$

$$5 + i_2 + i_2 - i_4 = 0$$

$$5 = i_4 - 2i_2$$

$$-\dot{i}_2 - \dot{i}_4 - \dot{i}_3 = 0$$

$$-\dot{i}_2 + \dot{i}_4 + \dot{i}_2 = 0$$

$$\dot{i}_4 = 0$$


$$V - \dot{i}_6 - \dot{i}_4 - \dot{i}_5 = 0$$

$$V - (\dot{i}_3 - \dot{i}_4) - \dot{i}_4 - \dot{i}_5 = 0$$

$$V + \dot{i}_2 - \dot{i}_5 = 0$$

$$V - (\dot{i}_2 - \dot{i}_4) + \dot{i}_2 = 0$$

Super Mesh Analysis.

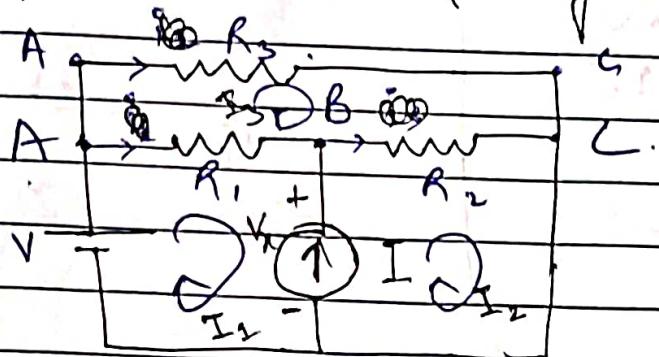

$$V - i_1 R_1 \neq 0.$$

~~$$-i_2 R_3 - i_3 R_2 - i_1 R_1 = 0.$$~~

~~$$i_3 R_2 \neq 0.$$~~

① Identify the loops / mesh

② Let I Amp Source is having the potential of V_x .

Applying KVL in loop ①

$$-V + (I_1 - I_3)R_1 + V_x = 0 \quad -\textcircled{1}$$


Applying KVL in loop ②

$$R_2(I_2 - I_3) - V_x = 0 \quad -\textcircled{2}$$

Adding eqn in ① & ②


$$(I_1 - I_3)R_1 + R_2(I_2 - I_3) = V \quad -\textcircled{3} \quad -\textcircled{1}$$

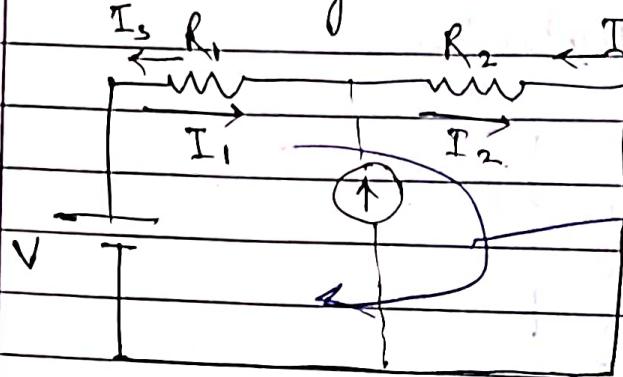Converting Current Source to form a Super mesh



Super mesh

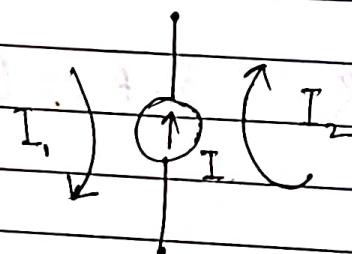
$$-V + R_1 (I_1 - I_3) + R_2 (I_2 - I_3) = 0$$



$$I_2 - I_1 = I \quad \text{--- (1)}$$

$$I_3 R_3 + (I_3 - I_2) R_2 + (I_3 - I_1) R_1 = 0 \quad \text{--- (III)}$$

Q

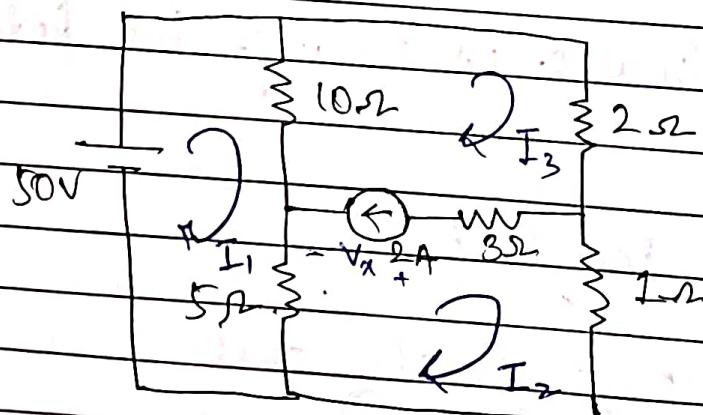

Find current the
5A resistance
by applying sup
mesh.

$$V_x - 5(I_2 - I_1) + I_2 - 3(I_2 - I_3) = 0$$

$$-V_{IL} - 10(I_3 - I_1) - 2I_3 = 0$$

$$10I_3 + 10I_1 + 5I_2 - 5I_1 + I_2 + 2I_3 + \cancel{8I_3} + \cancel{30I_1} = 0$$

$$-15I_1 + 6I_2 + \cancel{9}^{12} I_3 = 0 \quad \text{--- (1)}$$

$$\begin{aligned} I_3 - I_2 &= 2 \quad \text{--- (11)} \\ -15I_1 + 18I_3 &= 18 \end{aligned}$$

$$50 - 10(I_1 - I_3) - 5(I_1 - I_2) = 0$$

$$50 - 15I_1 + 10I_3 + 5I_2 = 0$$

$$50 - 15I_1 + 10I_3 + 15(I_3 - 2) = 0$$

$$50 - 15I_1 + 10I_3 + 5I_3 - 10 = 0$$

$$+15I_1 + 15I_3 = 40$$

$$15I_1 - 15I_3 = 40$$

$$15I_1 + 9I_3 - 18 + 15I_3 = 0 \quad 3I_3 = 52$$

$$15I_1 + 24I_3 = 18$$

$$15\left(I_1 - \frac{52}{3}\right) + 9I_3 = -22$$

$$\boxed{I_3 = \frac{52}{3}}$$

$$\boxed{I_1 = 50}$$

$$9I_1 - 52 - 15I_1 + 9I_3 - 18 + 9I_3 = 0 \quad \boxed{I_2 = \frac{46}{3}}$$


$$I_1 = \frac{60}{25}$$

$$18I_3 - 15I_1 = 18$$

$$\begin{array}{r} 58 \\ 3 \cancel{52}^{\cancel{3}} \end{array} \quad \begin{array}{r} 52 - 6 \\ 3 \end{array} \quad 3I_3 = 58$$

$$6 \times 58$$
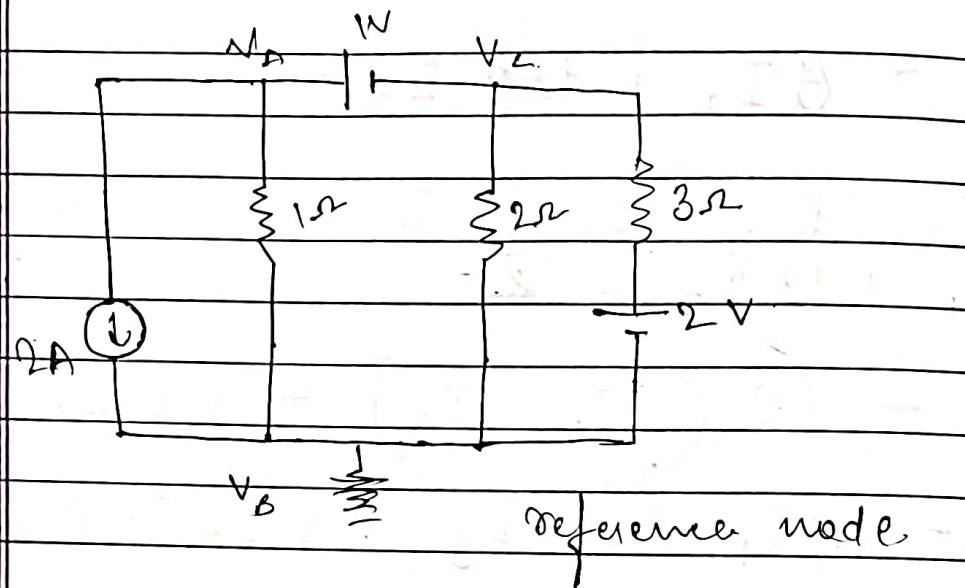
$$\begin{array}{r} 348 \\ 18 \\ \hline 520 \end{array} \quad \begin{array}{r} 18 \\ 18 \\ \hline 0 \end{array} \quad \begin{array}{r} 140 \\ 330 \\ \hline 25 \end{array}$$



Apply KCL at node \textcircled{A}

$$2 + \frac{V_A}{1} - i = 0 \quad \textcircled{1}$$


Apply KCL at node \textcircled{C}

$$\frac{V_C - 2}{3} + \frac{V_C}{3} + i = 0 \quad \textcircled{2}$$

Adding $\textcircled{1}$ & $\textcircled{2}$.

$$2 +$$

Supernode Analysis

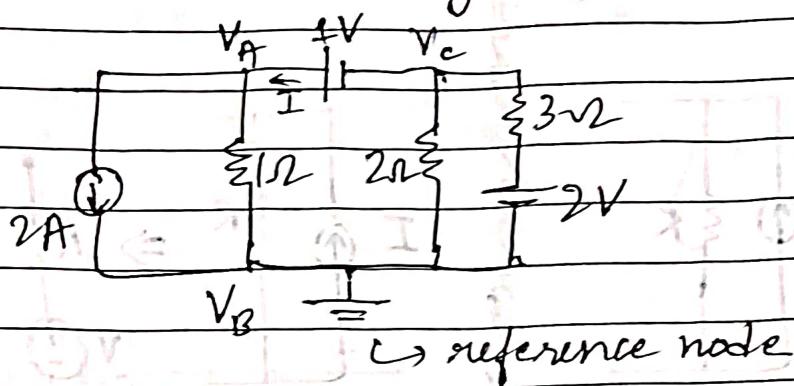

Applying KCL at node A

$$2 + \frac{V_A}{1} - I = 0 \quad \textcircled{1}$$


Applying KCL at node C

$$\frac{V_C - 2}{3} + \frac{V_C}{2} + I = 0 \quad \textcircled{2}$$

Add $\textcircled{1}$ & $\textcircled{2}$

$$2 + V_A + \frac{V_C - 2}{3} + \frac{V_C}{2} = 0$$

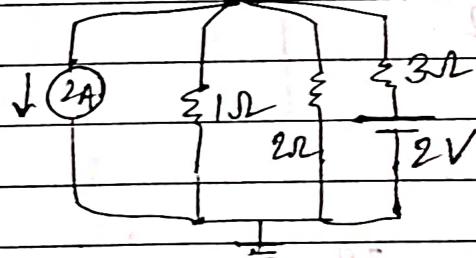
Making a Supernode, by eliminating voltage source



$$2 + \frac{V_A}{1} + \frac{V_C}{2} + \frac{V_C - 2}{3} = 0$$

5/9/24

Source conversions (?)

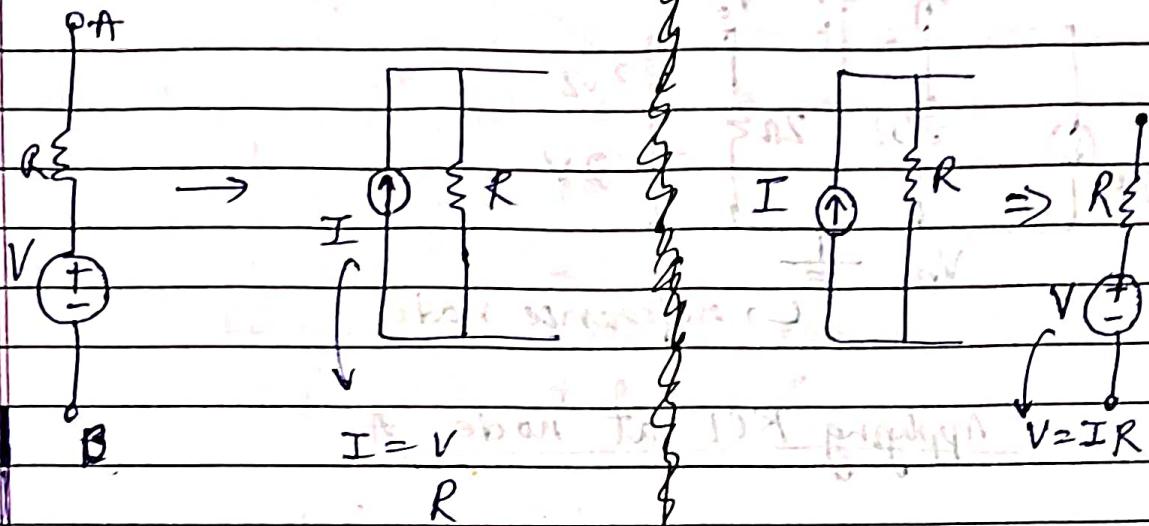


Classification of sources

- 1) Voltage source
 - 2) Current source
- Sources → Independent sources Sources → Dependent sources

(I) Independent sources

- 1) Voltage source

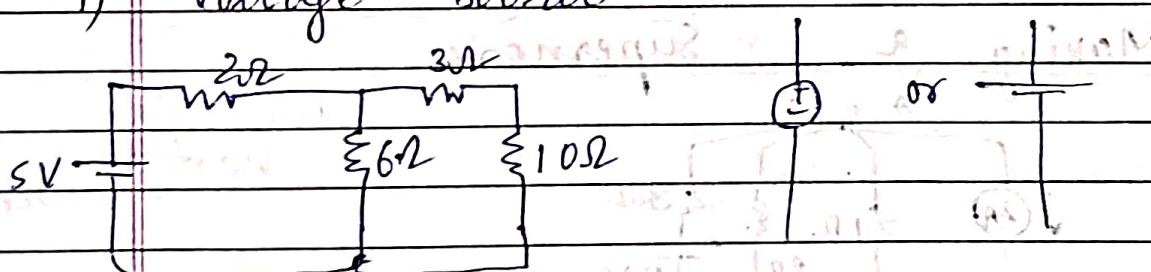

- 2) Current source



(II) Dependent sources


5/9/2y

1) Voltage dependent Voltage source (V_{DVS})

PAGE NO. _____
DATE _____


Voltage dependent voltage source. (V_{DVS}) (V_{CVS})

a)

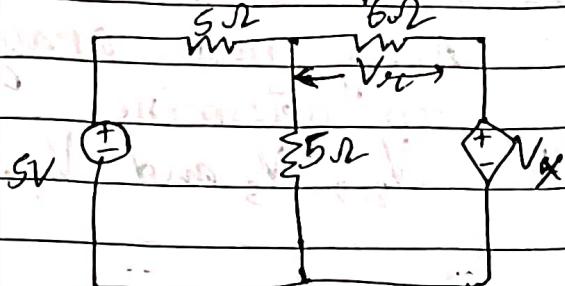

* Dependent \leftrightarrow diamond
diamond \rightarrow


b)

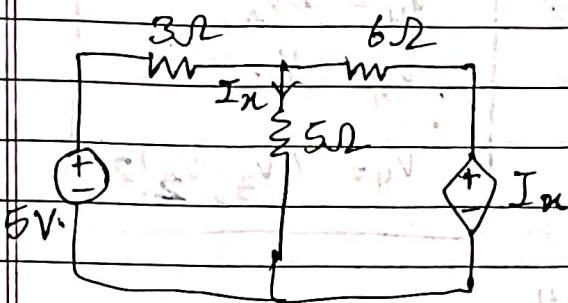

Current dependent voltage source (I_{DVS}) (I_{CeVS})

2) Dependent current source


a)

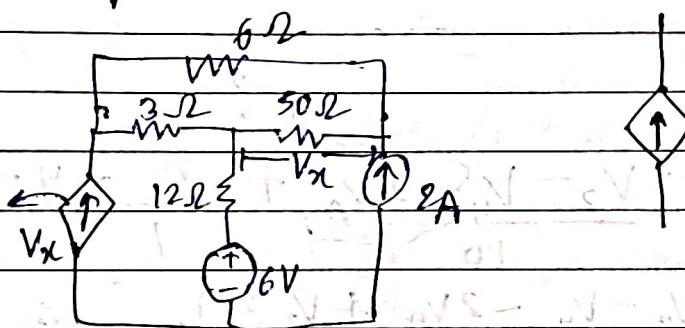


Voltage dependent current source (V_{DCS}) (V_{CICS})


b)

Current dependent current source

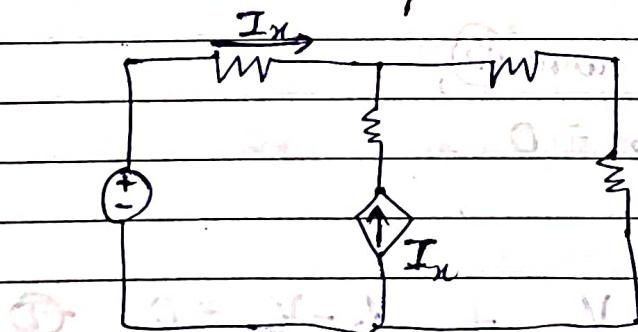

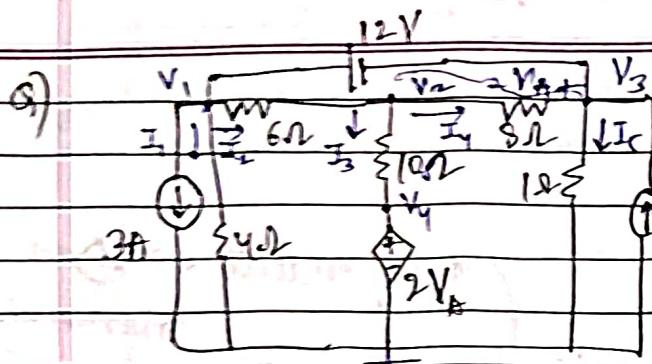

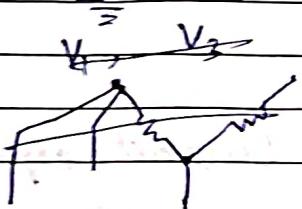Apply node analysis
to determine V_1 ,
 V_2 , V_3 and V_4 .



$$V_4 = 2V_A$$

$$V_A = \frac{V_2 - V_3}{2}$$

$$(V_4 = (V_2 - V_3)/2)$$

V_1, V_2, V_3

$$3 + I_1 + I_2 + I_3 = 4$$

~~$$\frac{V_2 - V_1}{10} + \frac{V_1}{4} + \frac{V_3}{1} = 4$$~~

~~$$3 + \frac{V_1}{4} + V_2 - V_1 - \frac{2V_A}{10} + \frac{V_3}{1} - 4 = 0$$~~

~~$$\frac{V_1}{4} + \frac{V_2 - V_1}{10} - 2V_A + \frac{V_3}{1} = 1 \quad (1)$$~~

~~$$3 + \frac{V_1}{4} + V_1 - V_2 + \frac{V_3}{1} = 12$$~~


Applying KCL at node ②,

$$3 + \frac{V_1}{4} + \frac{V_1 - V_2}{6} = 0$$

$$\frac{V_2 - V_1}{6} + \frac{V_2 - V_3}{8} + \frac{V_3 - V_1}{10} = 0 \quad (2)$$

Applying KCL at supernode:
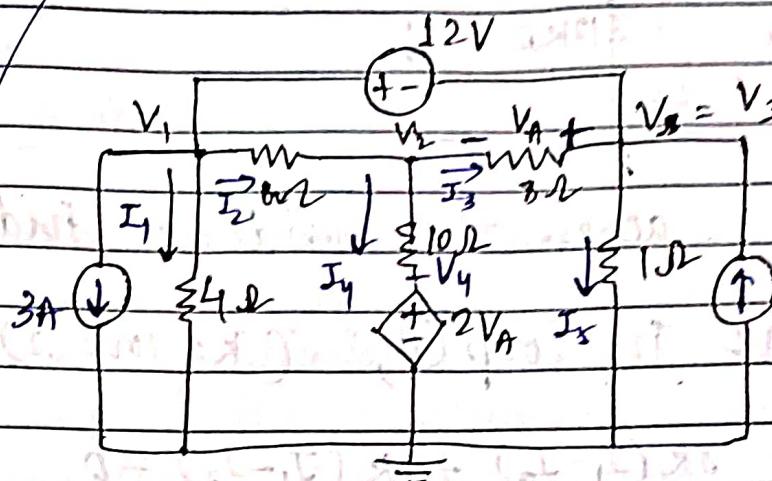
$$3 + \frac{V_1}{4} + \frac{V_2 - V_4}{10} + \frac{V_3}{1} - 4 = 0.$$



$$\begin{aligned} V_1 &= 9.62V \\ V_2 &= 1.45V \\ V_3 &= -2.32V \\ V_4 &= -7.54V \end{aligned}$$

→ by sig,

$$3 + I_1 + I_2 + I_3 = 4$$


{ used directly when you have done lots of question }

$$3 + \frac{V_1}{4} + \frac{V_2 - V_4}{10} + \frac{V_3}{1} = 4 \quad \text{---(2)}$$


$$0 = (V_1 - V_3) = 12 \quad \text{---(3)}$$

$$V_4 = 2V_A = 2(V_3 - V_2) \quad \text{---(4)}$$

can be simplified as:

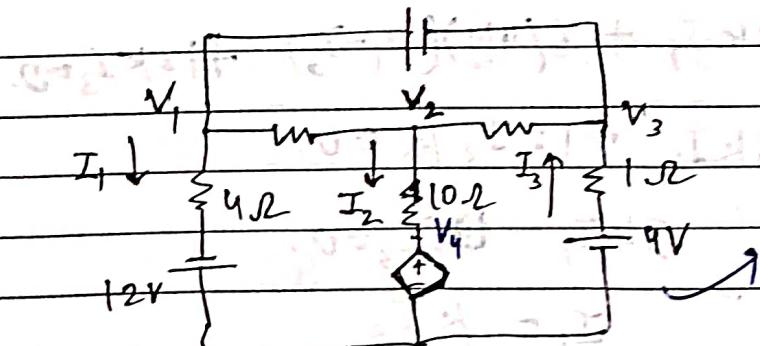

source conversions have been used

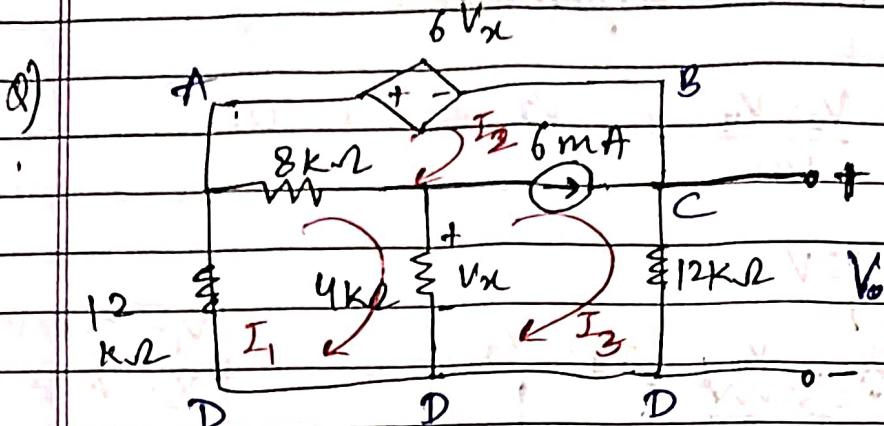

Find voltage across the resistance indicated.

Applying KVL in loop ①, ($K = 1000 \Omega$)

$$① 12K(I_1) + 8K(I_1 - I_2) + 4K(I_1 - I_3) = 0$$

$$② I_2 - I_2 = 6 \text{ mA} \quad \text{--- } ②$$

$$\cancel{6m + 12K(I_3) - 4K(I_3 - I_1) = 0}$$

Applying KVL in supermesh ABCDA,

$$12KI + 6V_x + 12K(I_2) = 0. \quad ③$$

$$V_x = 4K(I_1 - I_3)$$

solving,

$$④ 24KI - 8KI_2 - 4KI_3 = 0.$$

$$I_2 = I_3 - 6 \text{ mA}$$

$$12KI_1 + 6(4K)(I_1 - I_3) + 12KI_3 = 0.$$

$$36KI_1 - 12I_3 / 2 = 0,$$

$$3KI_1 - 2KI_3 = 0,$$

$$I_1 = \frac{KI_3}{3K}.$$

$$\frac{8K(KI_3)}{3K}$$

$$-8K(I_3 - 6 \text{ mA})$$

$$-4KI_3 = 0.$$

$$4K - 4KI_3 = 0$$

$$I_3 = 12 \text{ mA}$$


$\Rightarrow I_1 = 4 \text{ mA}$, $I_2 = 6 \text{ mA}$. and
 $I_3 = 12 \text{ mA}$.

$$\therefore V_o = 12 \times 2(12 \text{ mA}) = 144 \text{ V.}$$


18/9/24

SUPERPOSITION THEOREM

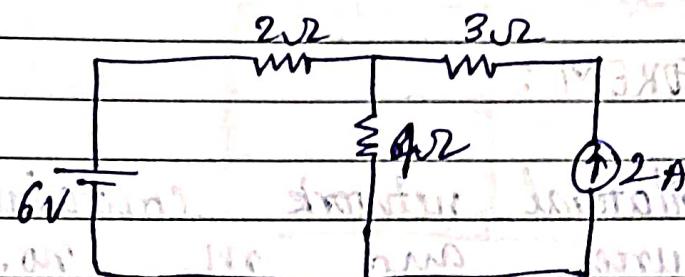In a linear bilateral network containing n no. of sources, the current through a particular element can be calculated as the algebraic sum of effect of all the sources considering one source at a time and replacing all the other sources by their internal resistances.



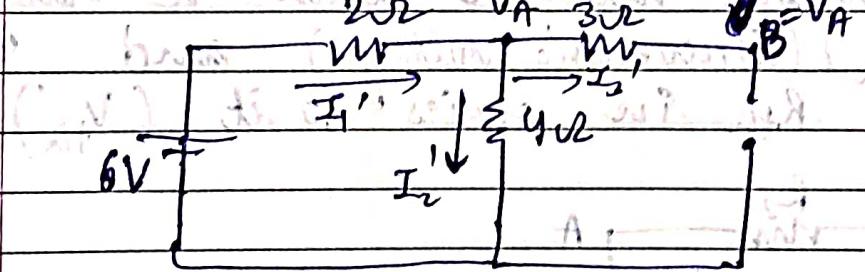i) Considering 6V source (internal resistance of source = ∞)




Points A and B are at same potential

$$I'_1 = 1 \text{ A}$$

$$- I'_2 = 1 \text{ A}$$

$$I'_3 = 0 \text{ A}$$

2) Considering 2A source

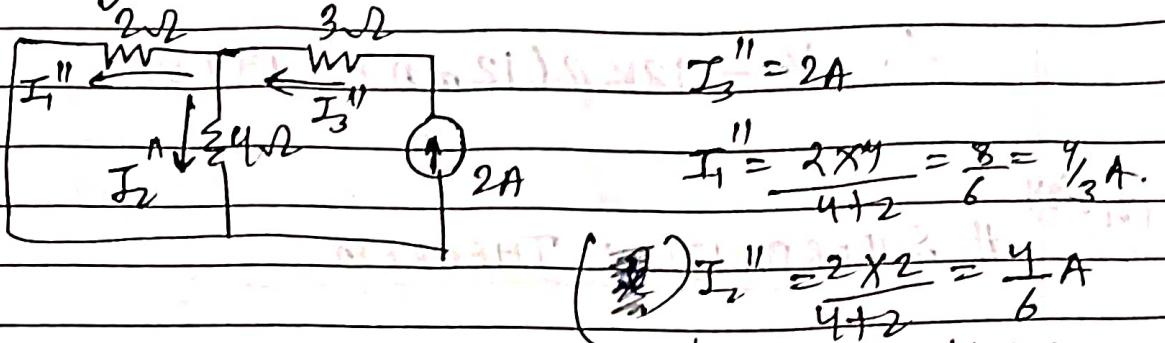

using alternative method \rightarrow current division rule.


Solving, $I_1 = I_1' - I_1'' = 1$ (badly written)

and $I_2 = I_2' + I_2'' = 2$ (with some calculation)


$I_3 = I_3' - I_3'' = 2$ (current division)

JHEVENIN'S THEOREM:

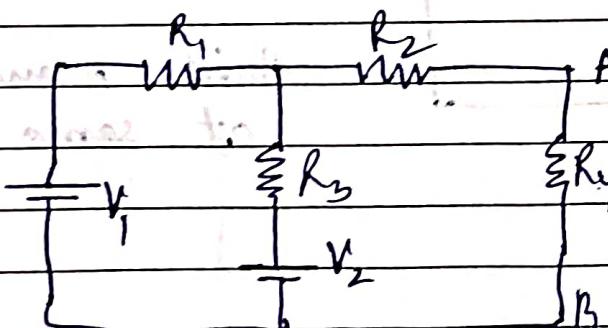In a linear bilateral network containing n no. of sources and m no. of elements, the current through a particular element can be calculated by replacing whole network with a voltage source, (V_{th}) (Jhevenin's voltage) and a resistance R_{th} in series to it. (R_{th}).




- 1) Open circuit the load resistance

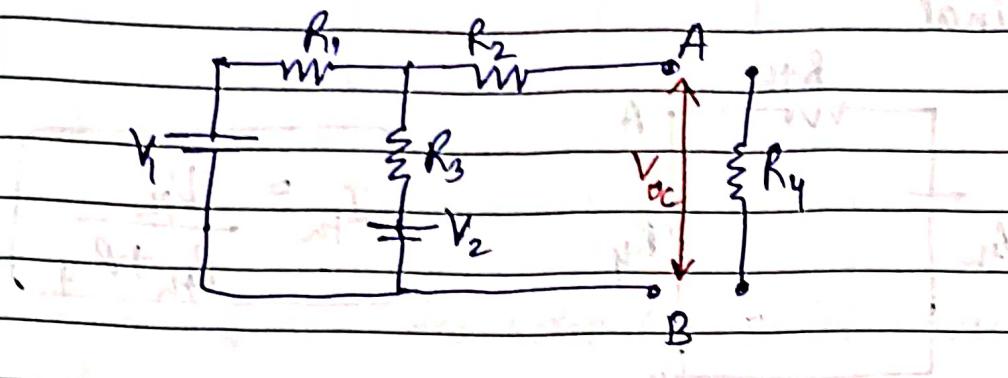


Then find open circuit voltage at the open ends, $V_{oc} \Rightarrow V_{th}$

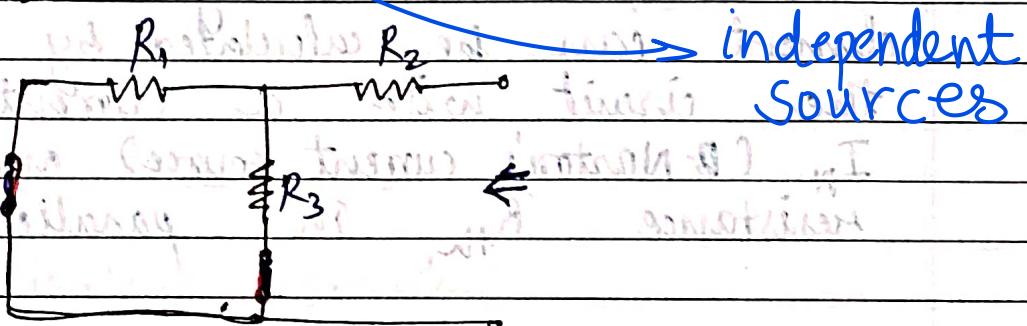- 2) Find the internal resistance of the circuit as seen from open end, by replacing all the sources by their internal resistances




$$R_{th} = (R_1 || R_3) + R_2$$

- 3) Draw Thevenin's equivalent

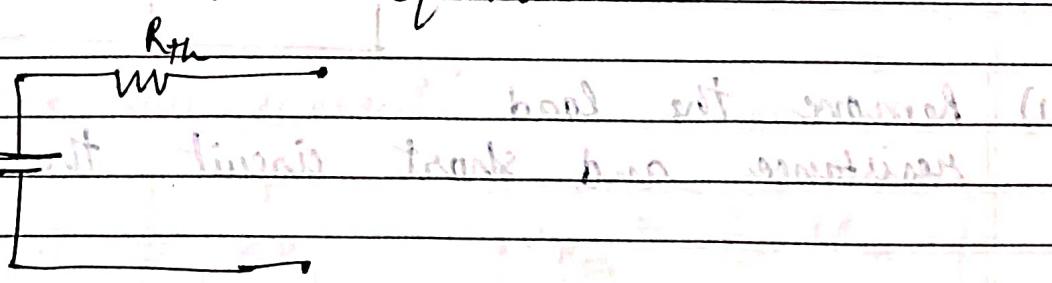

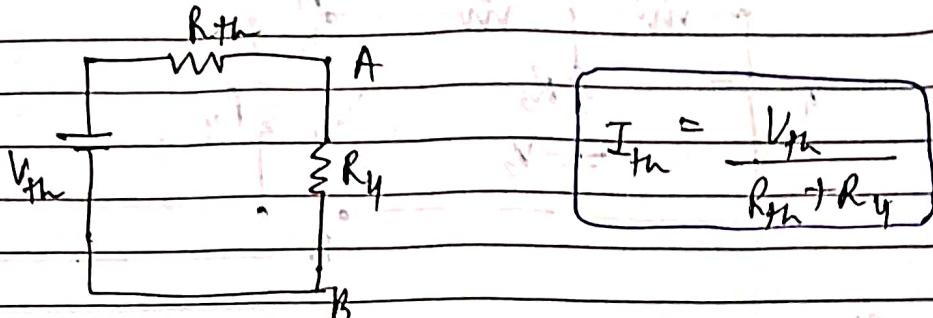- 4) Connect the load resistance at the open terminal




$$I_{th} = \frac{V_{th}}{R_{th} + R_L}$$


NORTON'S THEOREM

In a linear bilateral network containing n no. of sources and m no. of elements, current through a particular element can be calculated by replacing the circuit with a current source I_N (B:Norton's current source) and a resistance R_{th} in parallel to it (I_N)

8 steps:

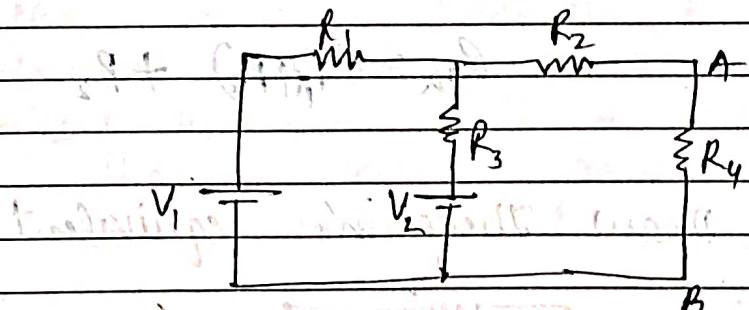

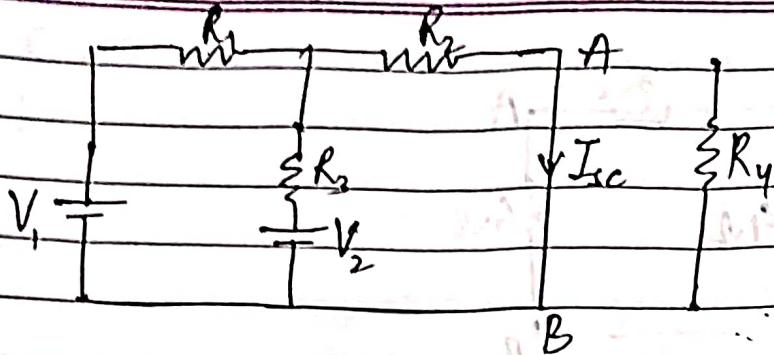
- 1) Remove the load resistance and short circuit the open end



then find I_{sc} (short circuit current) through it.


$$\text{This } I_{sc} = I_N$$

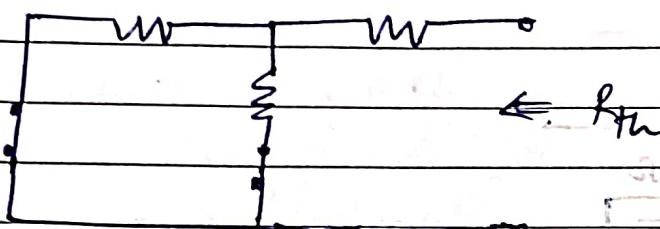- 2) Find R_{th} by replacing all the sources with their internal resistance as seen from the open end.




$$R_{th} = (R_1 + R_3) + R_2$$


- 3) Draw Norton's Equivalent

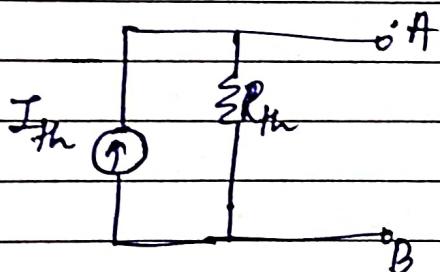

- 4) find the load current

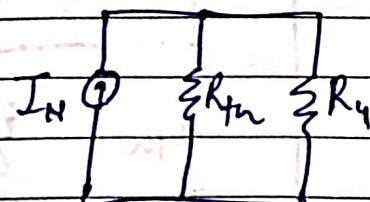

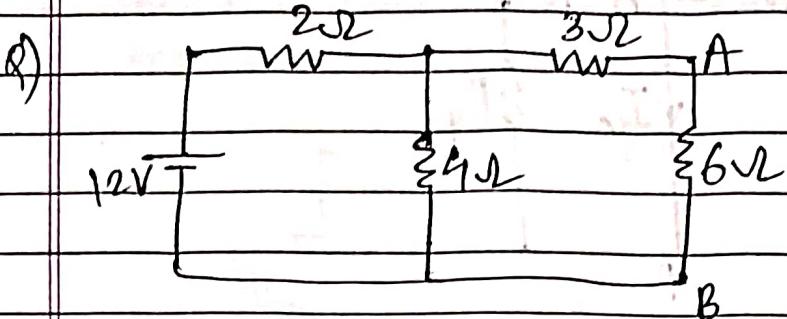
$$I_{R_4} = \frac{I_N \times R_N}{R_{th} + R_4}$$




1) $V_{AB} = 8V$

2) $R_{th} = \frac{13}{3}\Omega$

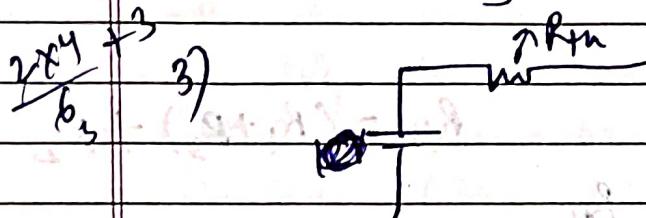

4) $I = \frac{8}{6}A = \frac{8}{10.3}A = 24A$

$\frac{13}{3} + 6$


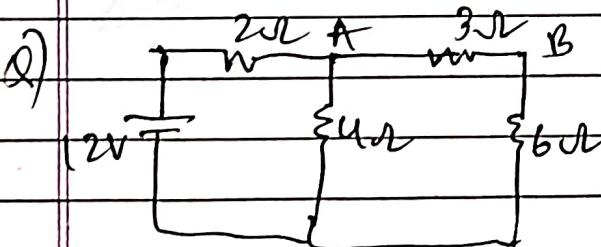


1) $V_{th} = 8V$

$V_{th} = 8V$

2) R_{th}

$$R_{th} = \frac{8}{6} + 6 \\ = \frac{44}{6} \Omega$$

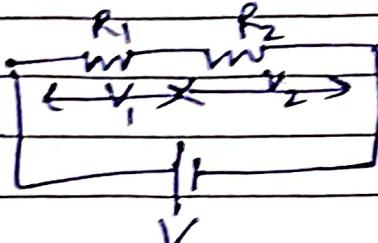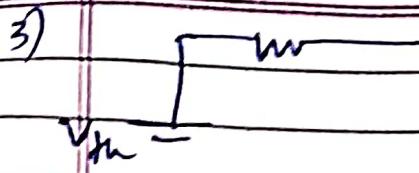


Assignment 2

Q3) $-2W, -49.09mW, -200\mu W$

$$V_1 = \frac{V \times R_1}{R_1 + R_2}, I_a = \frac{V}{R_2}$$

Q4) $-20W, 100W, -80W$

~~$V = \frac{V_1 R_2}{R_1 + R_2}$~~

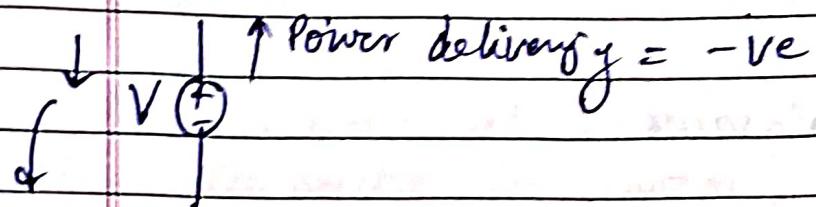

Power absorbed = +ve.

5) Current = 707 mA

6) $-960W, 1920W, -1920W, 960W$

7) 14.4V, 34.56 mW

8) 7.5V

9) 4 nodes,

7 elements, 6 branches

10) 4 nodes, 5 elements, 5 branches

11) $-49A$

12) 4.5 kW

13) $i_1 = -250 \text{ mA}$

15) 8.933 V, 10.65 W

16) $I_x = 6.639A$

17) 3.257W

18) $i_x = 1.4A$

19) $I = 3.307 \text{ mA}$


20) $V_{th} = 8V, R_{th} = 10k\Omega$

23/9/2024

PAGE NO. _____
DATE _____


Unit - 2

AC Circuits

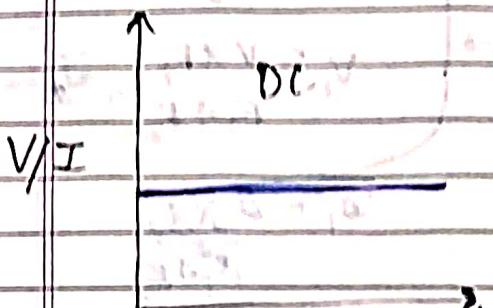

Both directions and magnitude are constant.

Magnitude remains same

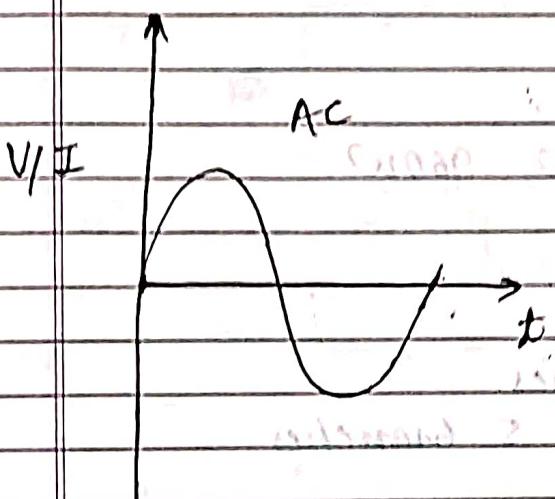

Both magnitude and directions changes

Generation of AC

→ Here Faraday's law of electromagnetic induction is applied.


When a conductor cuts the magnetic field or a flux linking with the conductor changes w.r.t time, an emf is induced in the conductor.

$$E = -N \frac{d\phi}{dt}$$

"direction of emf produced is such that it opposes the cause which is creating it." — (Lenz's law)

There are two ways in which conductor can link with flux.

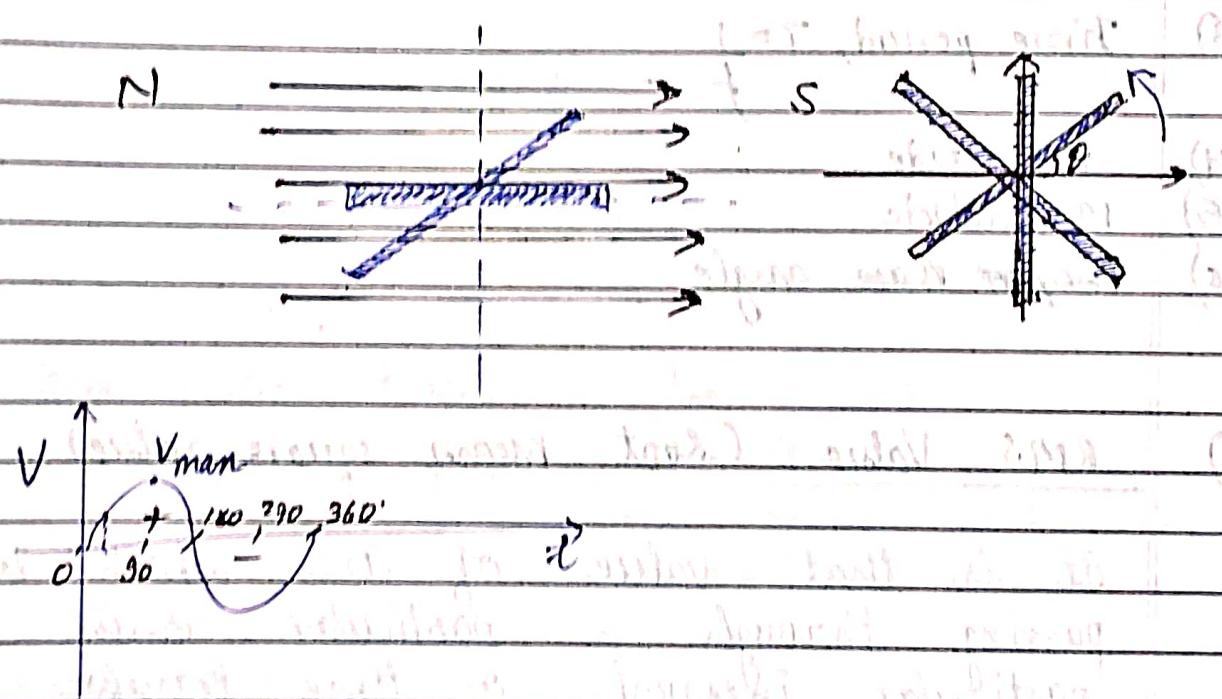- (i) conductor at rest, field changing
- (ii) conductor in motion, field at rest.



$$E = -N \frac{d\phi}{dt}, \quad \phi = \phi_m \cos \omega t$$

$$\omega = wt, \text{ rad/sec} \quad \frac{d\phi}{dt} = -\phi_m w \sin \omega t$$

$$\therefore E = N\phi_m w \sin wt$$

 E_{max} if $E = V$,

$$V = V_{max} \sin wt$$

$$V_{max} = V = N\phi_m w$$

$$I = I_m \sin wt$$

Instantaneous values

- 1) Cycle
- 2) frequency = no. of cycles in 1 sec; $f = \frac{1}{T}$.
- 3) Time period, $T = \frac{1}{f}$
- 4) Amplitude
- 5) Magnitude
- 6) Phase angle.

1) RMS Value (Root mean square value)

It is that value of DC which when passing through a particular circuit for a particular interval of time transfers same amount of heat as transferred by AC in same circuit when flowing for same interval of time.

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

No. where
wave form
wave
is other
than
sine
wave

$$\left. \begin{aligned} V_{rms} &= \int_0^{2\pi} (V_m \sin \omega t)^2 dt \\ &= \frac{1}{2} \text{Area under the curve}^2 dt \\ &\quad \text{Base length} \end{aligned} \right\}$$

2) Average value

It is that amount of DC which transfers same amount of charge as transferred by AC flowing through same circuit flowing for same interval of time.

$$V_{av} = \frac{2V_m}{\pi}$$

$$\Rightarrow V_{av} = 0.637 V_m$$

$$V_{av} = \int_0^T V_m \sin \omega t dt$$

$$3) \text{Form factor } = \frac{V_{rms}}{V_{av}} = \frac{V_m/\sqrt{2}}{2V_m/\pi} =$$

$$FF = 1.11$$

Same fixed values for a sine wave.

4) Crest factor

$$CF = \frac{\text{Max value}}{\text{RMS value}} = \frac{V_m}{V_m/\sqrt{2}}$$


$$CF = \sqrt{2} = 1.414$$

25/8/28

(V = fixed quantity)

PAGE NO.	
DATE	


1) AC through pure resistance:

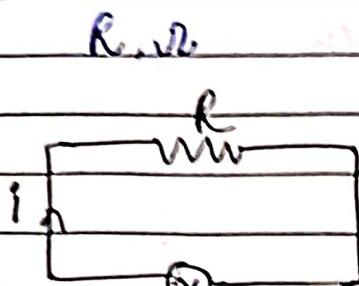

$$V = V_m \sin \omega t$$


$$i = I_m \sin \omega t$$

$$I_m = \frac{V_m}{R}$$

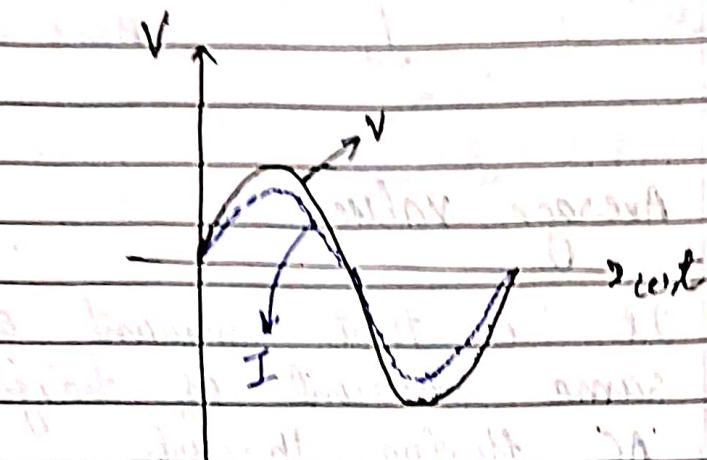


→ Here, voltage and current are in same phase.

→ Phasor diagram:

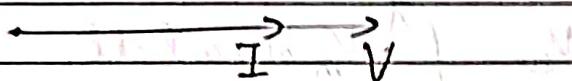

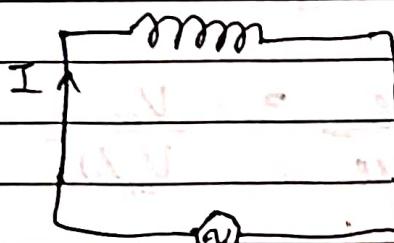2) AC through pure inductor L, Henry (H)

Inductance is the property of material due to which it opposes the rate of change of current.



$$V = V_m \sin \omega t$$

Property to oppose rate of change of currents
 $\frac{di}{dt}$




Phase difference
b/w V and I
 $= 90^\circ$.

Current lags behind voltage by a phase of 90° .


$$V = V_m \sin \omega t \quad (I = I_m \angle -90^\circ)$$

$$I = I_m \sin (\omega t - 90^\circ)$$

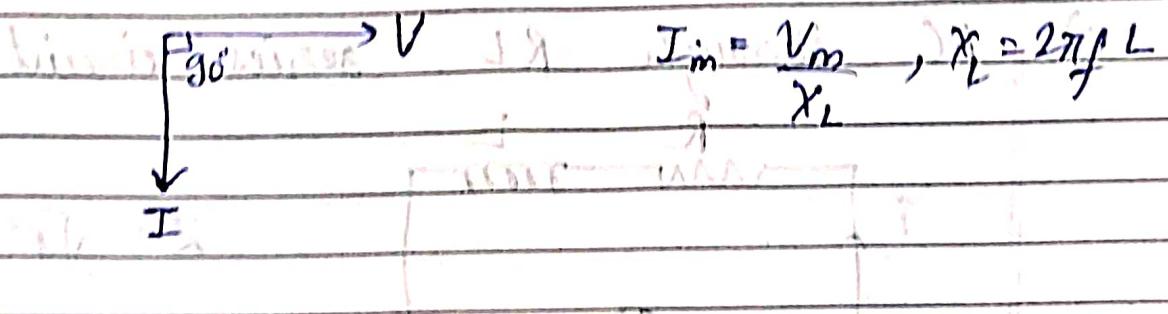


3) AC through Pure capacitance

Capacitance, Farad, F

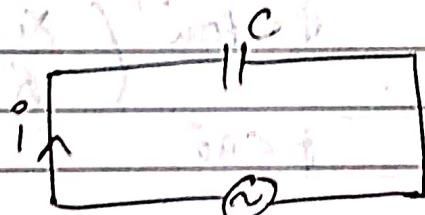

Capacitance is the property due to which capacitor opposes rate of change of voltage.

$$\frac{dV}{dt}$$

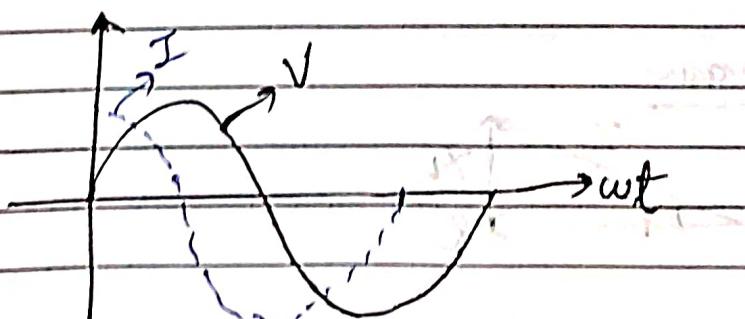


Current will lead the voltage by 90° .

$$V = V_m \sin \omega t$$

$$I = I_m \sin(\omega t + 90^\circ)$$


$$I = I_m \angle 90^\circ$$

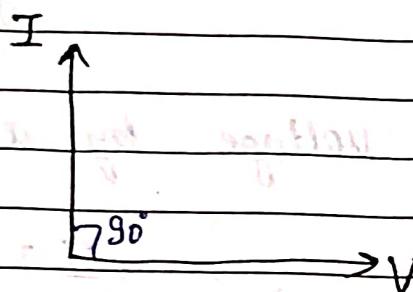


$$I_m = \frac{V_m}{X_C}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

1) AC through RL series circuit

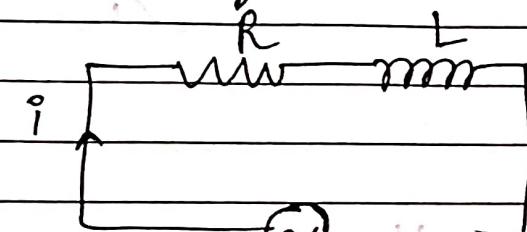
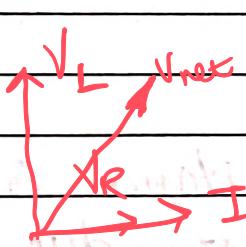
$$Z = \sqrt{R^2 + X_L^2} \text{ } \Omega$$




$$V_{net} = V_m \sin \omega t$$

$$I = I_m \sin(\omega t - \phi)$$

$$\phi = \tan^{-1} \left(\frac{X_L}{R} \right)$$

$$\phi < 90^\circ$$

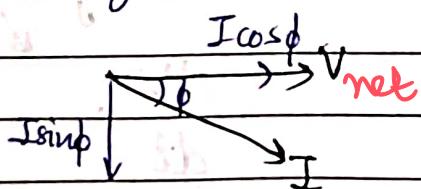current lags behind voltage by an angle ϕ , $\phi < 90^\circ$.



Impedance diagram

